

ENR-325/325L Principles of Digital Electronics and Laboratory



Course Syllabus and Discussion

This introductory course provides a comprehensive foundation in Digital Electronics, starting with basic principles and progressing to digital design and system applications.


Through a combination of lectures, hands-on labs, and a final project, students will develop the skills to design, implement, and test basic digital systems and IoT prototypes. The course incorporates the use of digital logic simulation software and emphasizes the engineering design process and ethical considerations.

EP1: Digital and Information Systems

- The learning curve from EE to IC.
- Digital abstraction.
- Information theory and its application.

The learning curve from EE to IC

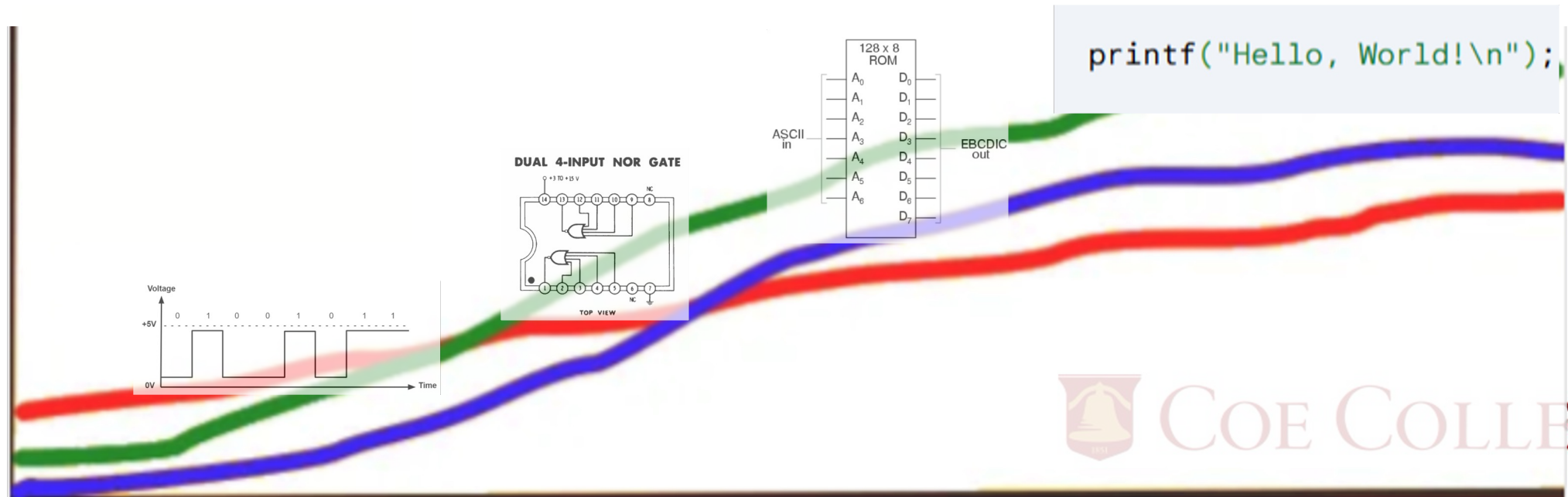
Presented learning curve from many EE/IC/CE courses.



The learning curve from EE to IC


Actual learning curve to (part of the) industry.

```
printf("Hello, World!\n");
```

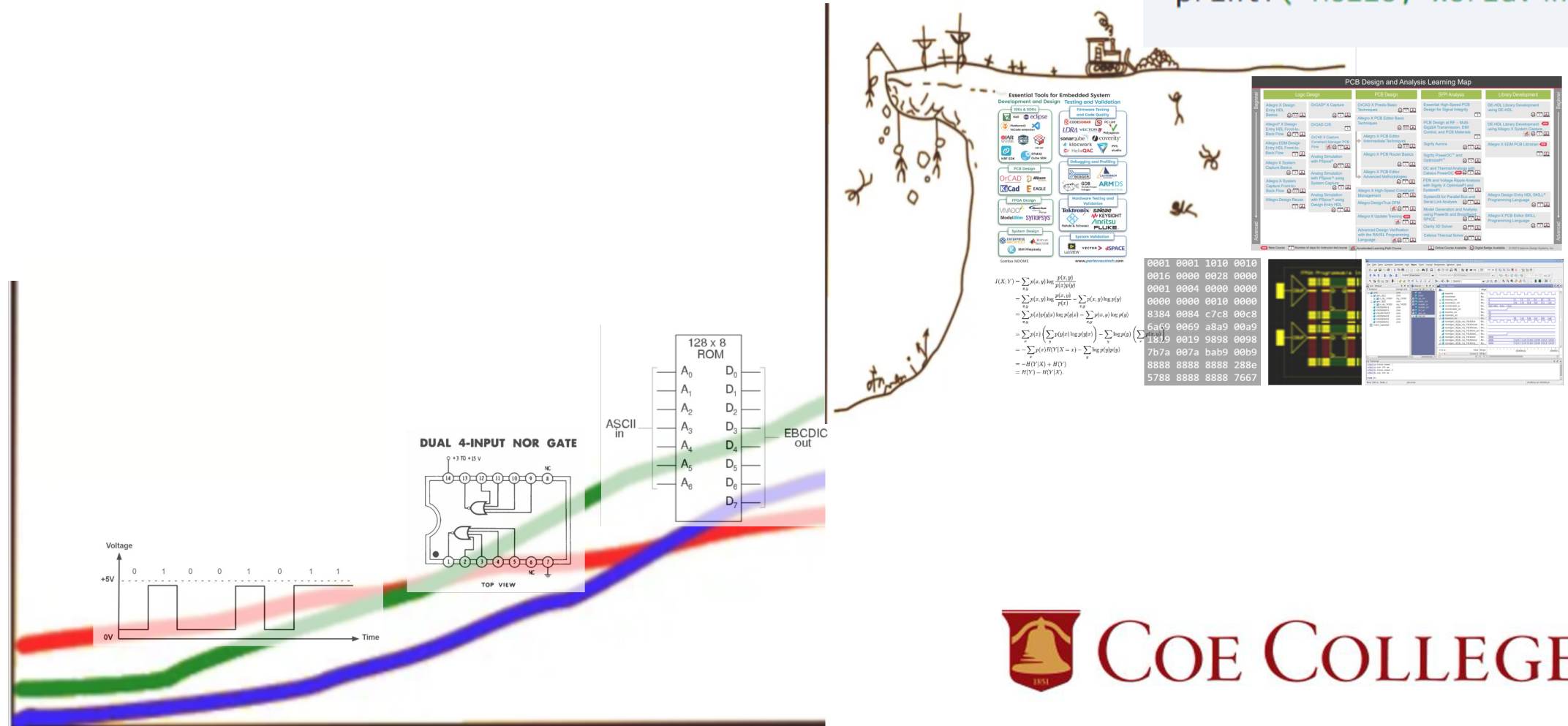

The learning curve from EE to IC

The goal of this course:

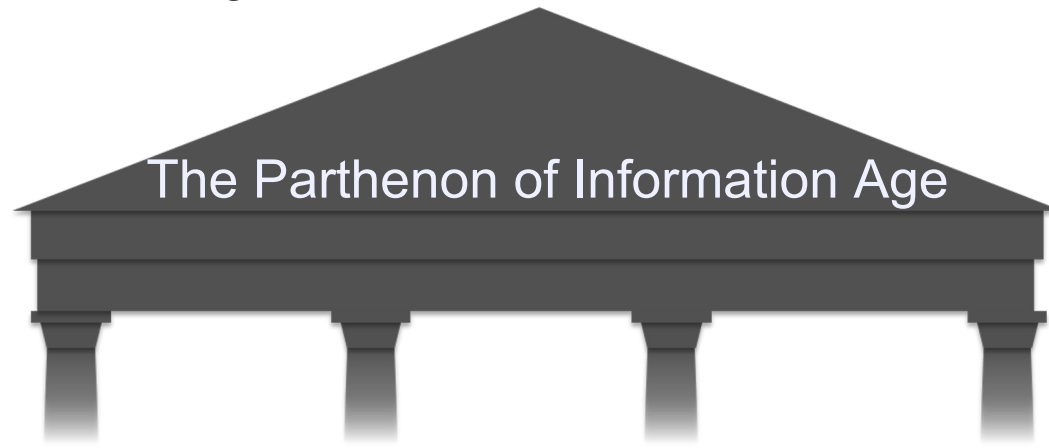

The Parthenon of Information Age



Theory



Hardware



Software



System integration



COE COLLEGE®

Why go digital? – the MATH/CS version (theory)

Symbolic logic



Computer
arithmetic



Modern day CS

THE MATHEMATICAL ANALYSIS

OF LOGIC,

BEING AN ESSAY TOWARDS A CALCULUS
OF DEDUCTIVE REASONING.

BY GEORGE BOOLE.

Ἐπικοινωνοῦσι δὲ πᾶσαι αἱ ἐπιστῆμαι ἀλλήλαις κατὰ τὰ κοινά. Κοινὰ δὲ λέγω, οἷς χρῶνται ὡς ἐκ τούτων ἀποδεικνύντες· ἀλλ' οὐ περὶ ὧν δεικνύουσιν, οὐδὲ ὃ δεικνύουσι.

ARISTOTLE, *Anal. Post.*, lib. I. cap. XI.

CAMBRIDGE:
MACMILLAN, BARCLAY, & MACMILLAN;
LONDON: GEORGE BELL.

1847

gutenberg.org

“The starting point of digital circuit design.”

A SYMBOLIC ANALYSIS
OF
RELAY AND SWITCHING CIRCUITS

by

Claude Elwood Shannon
B.S., University of Michigan
1936

Submitted in Partial Fulfillment of the
Requirements for the Degree of
MASTER OF SCIENCE
from the
Massachusetts Institute of Technology
1940

dspace.mit.edu



<https://www.juggle.org>



COE COLLEGE

Shannon's juggling bot: <https://www.youtube.com/watch?v=tXU3EPg2cgA>


Why go digital? – the Computational/IC version (hardware)

Charles Babbage's
Difference Engine, 1820s




Science Museum
London, UK

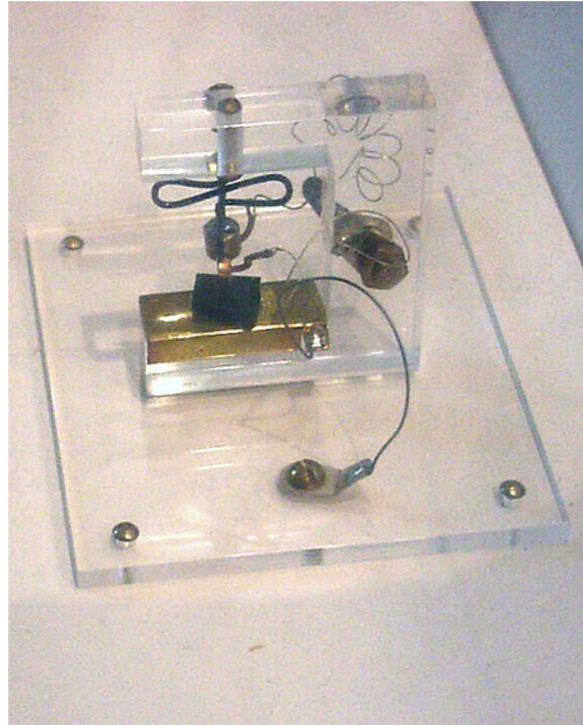A replica of the world's
first transistor, 1947




National Air and Space Museum
Washington, DC, USA

The IAS computer, 1952

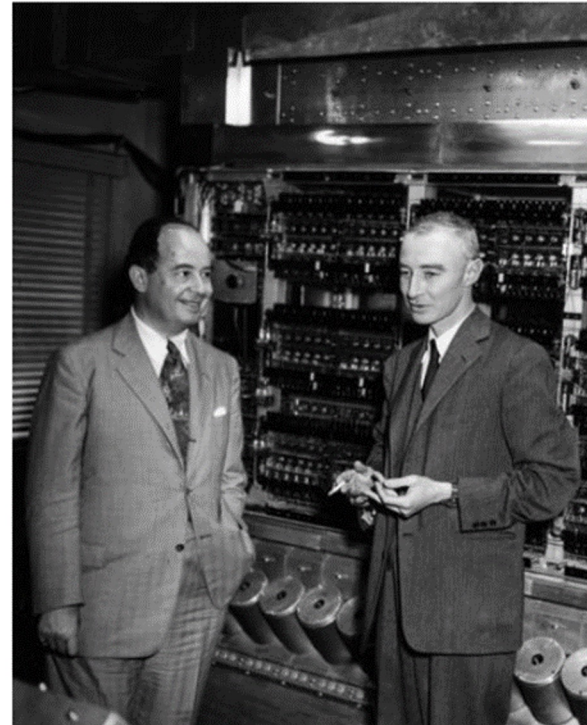

www.computerhistory.org

Intel 80186, 1982

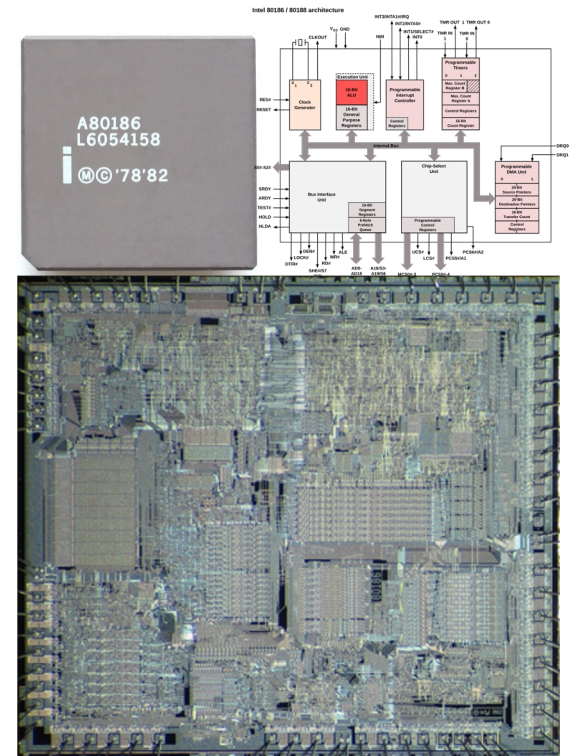


wikipedia.org/wiki/Intel_80186




Why go digital? – the Phys/MicroE version (application)

Film camera vs CCD camera

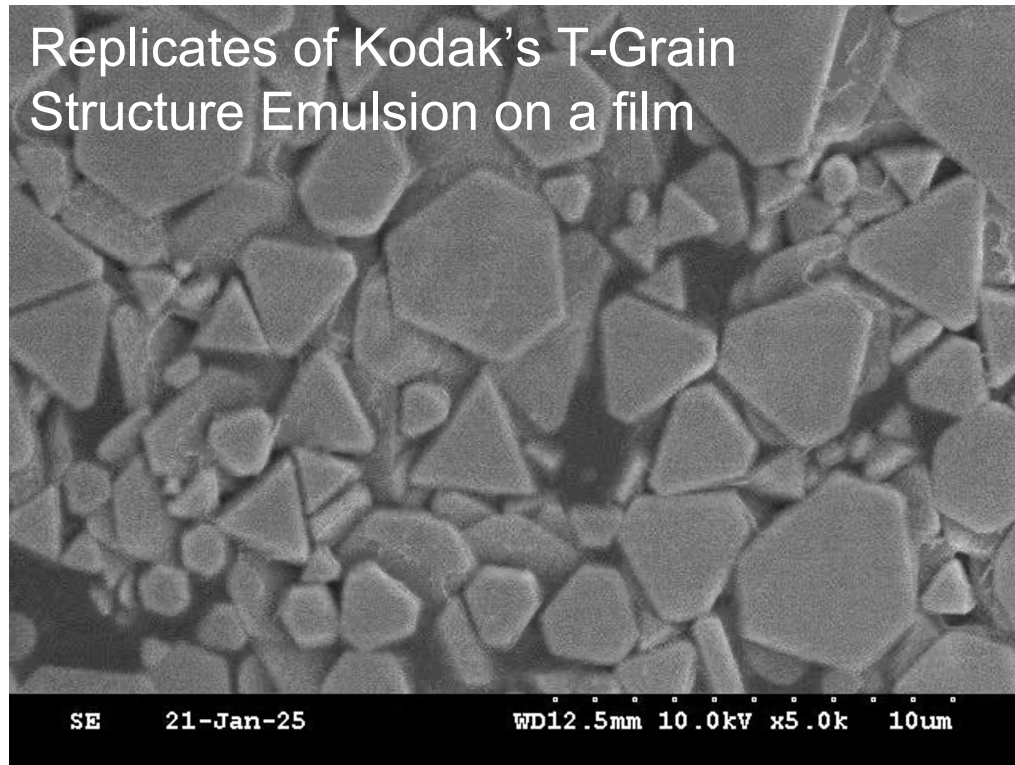

lightlenslab.com

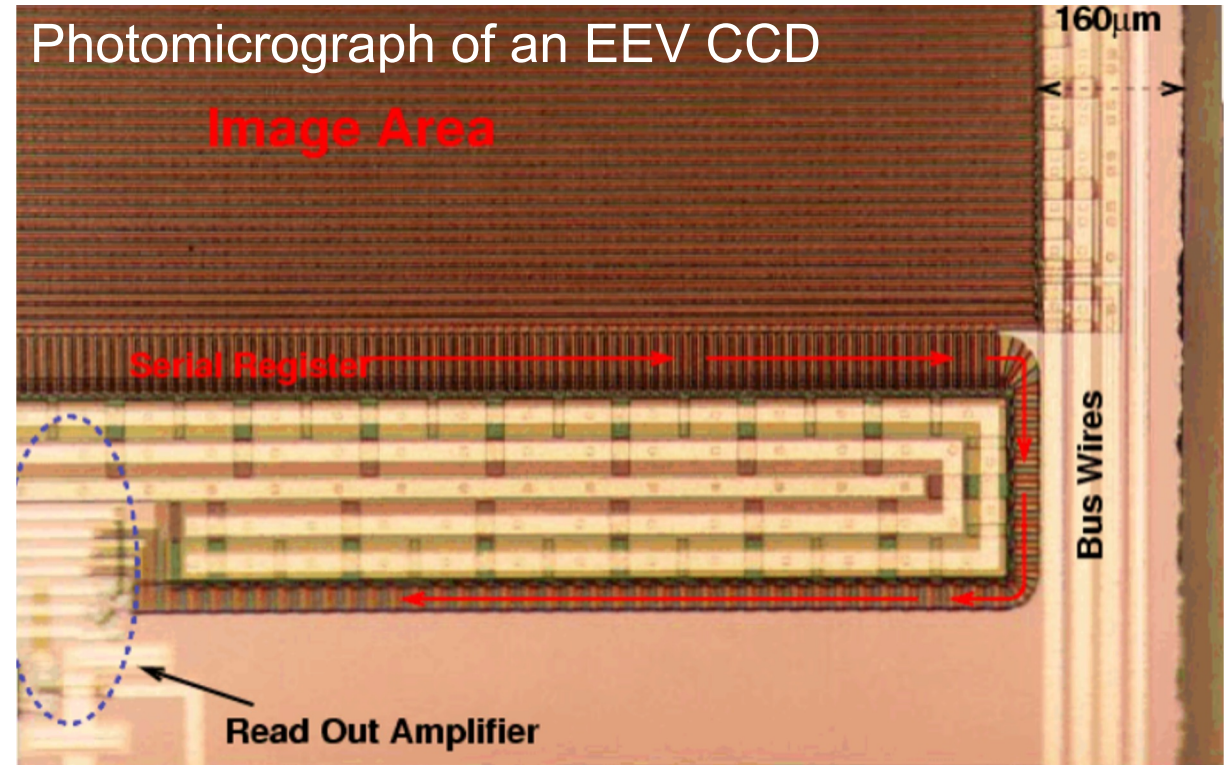

<http://spiff.rit.edu/classes/phys445/lectures/ccd1/ccd1.html>




COE COLLEGE®

Why go digital? – the Phys/MicroE version (application, continued)

Film vs CCD by Liam Kix

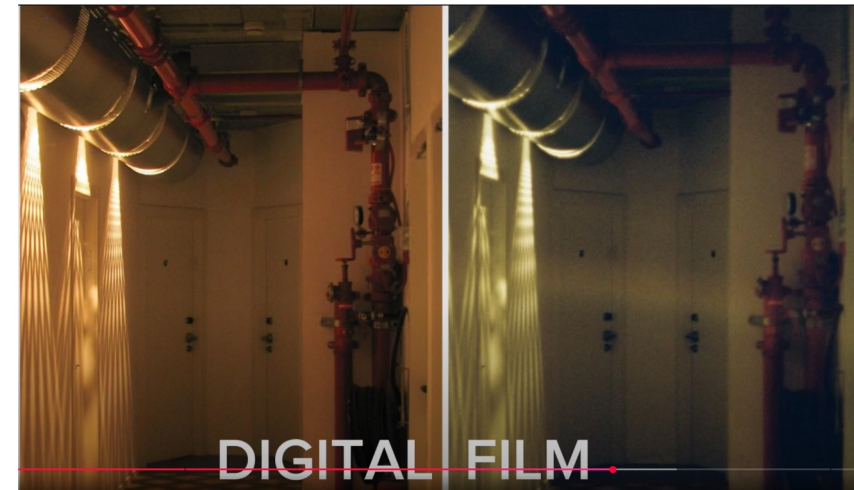https://youtu.be/YBT7PZrjKvw?si=Fgy_3RfV8aZ65oU-



COLLEGE®

Why go digital? – the EE version

Because it's lazy and easy.

From analog circuits we learn:

LCA, KVL, KCL, node


For linear circuits: superposition, Thevenin, Norton

So instead of lumping matter, we will lump **signal values**, which will lead to the **digital abstraction**.

Class reflex: digital good

- Let's share experience with boons we got from the digital age.

A quick detour to circuits analysis:

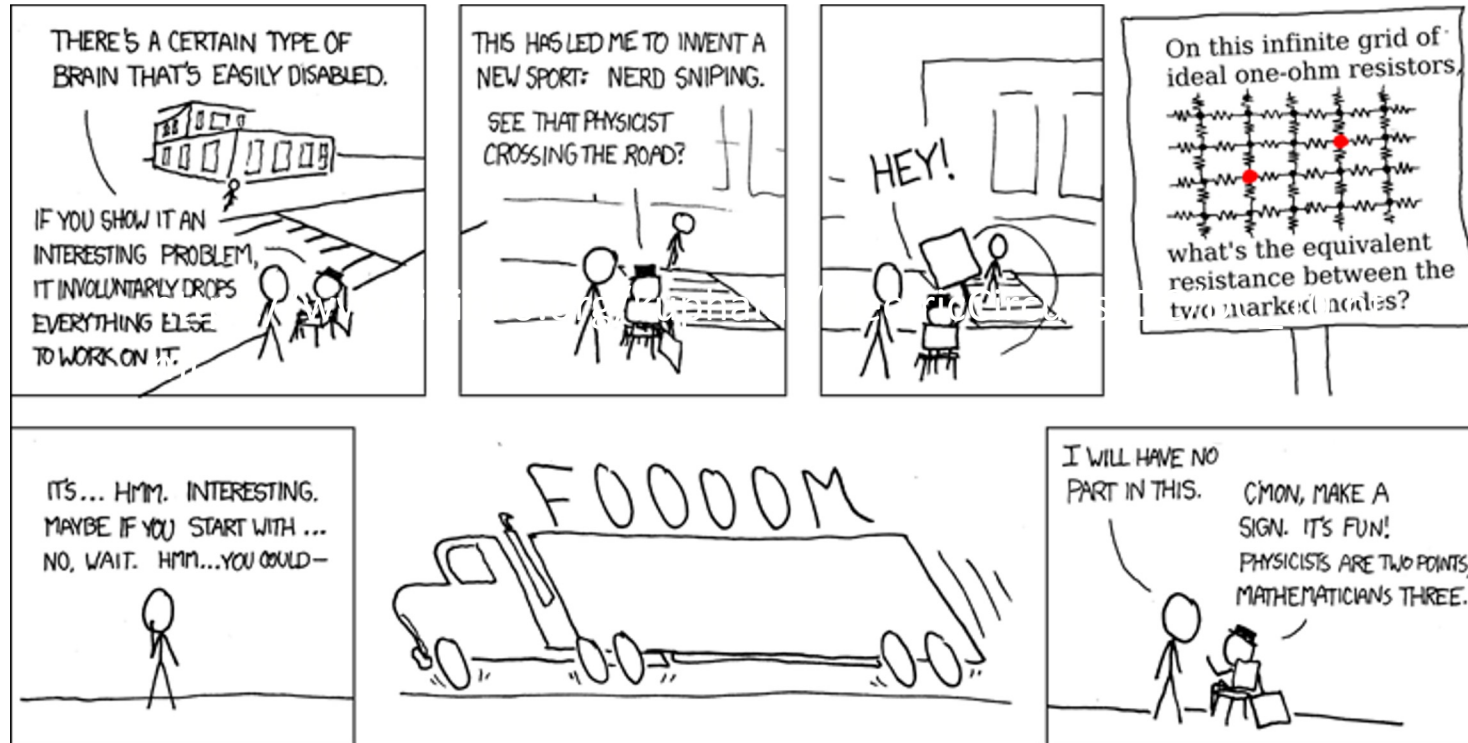


<https://xkcd.com/356/>

A place to refresh your memory:

https://www.ibiblio.org/kuphaldt/electricCircuits/DC/DC_10.html

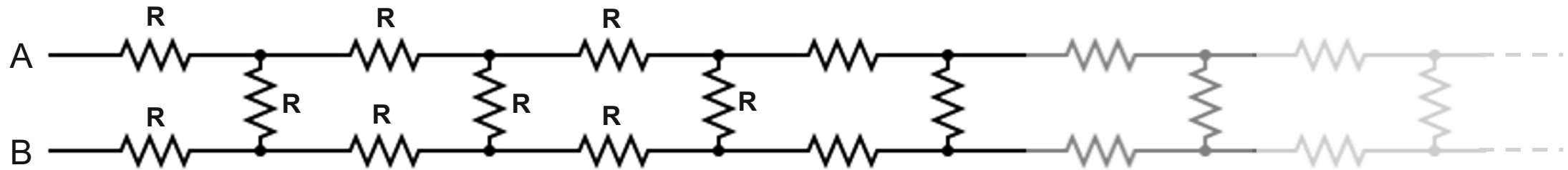
Let's do an infinite resistor ladder puzzle



To get: equivalent resistor between point A and B, if the ladder goes infinite.


Why go digital? – the EE version

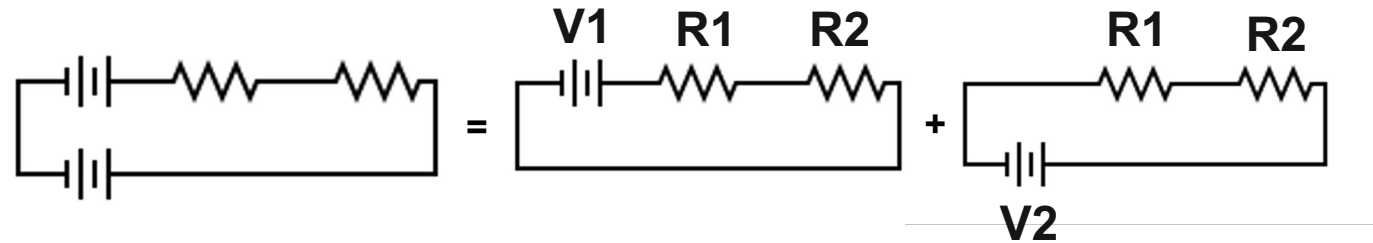Your typical electric circuits about superposition is like:




The classical demo in telecommunications: noise resistance

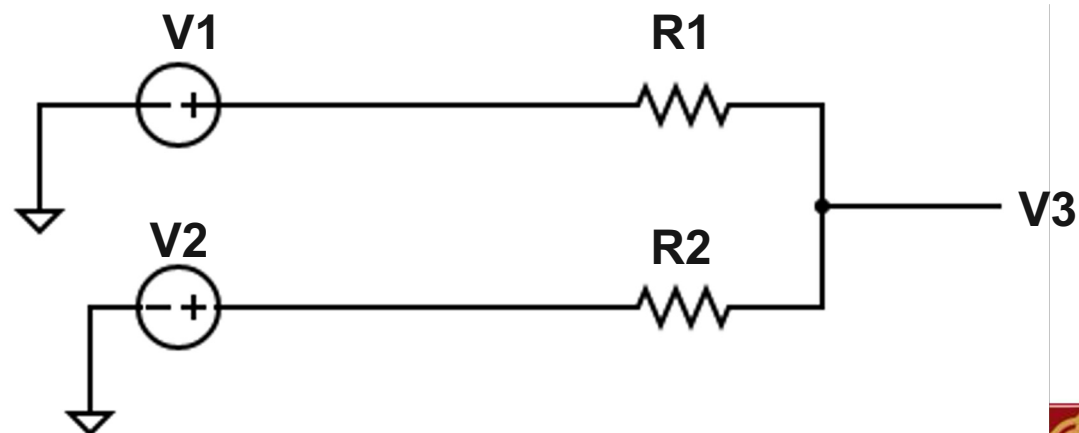Telecommunication: don't care about current but measure the voltage drop only:



Why go digital? – the EE version

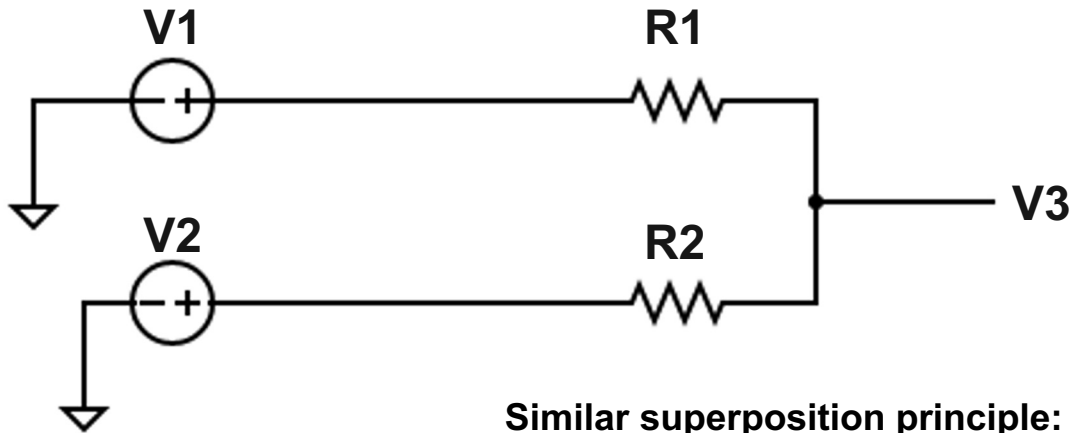The classical demo in telecommunications: noise resistance




Similar superposition principle:

$$V3 = V1 \frac{R2}{R1+R2} + V2 \frac{R1}{R1+R2}$$

© 2021 Circuit Diagram

Why go digital? – the EE version

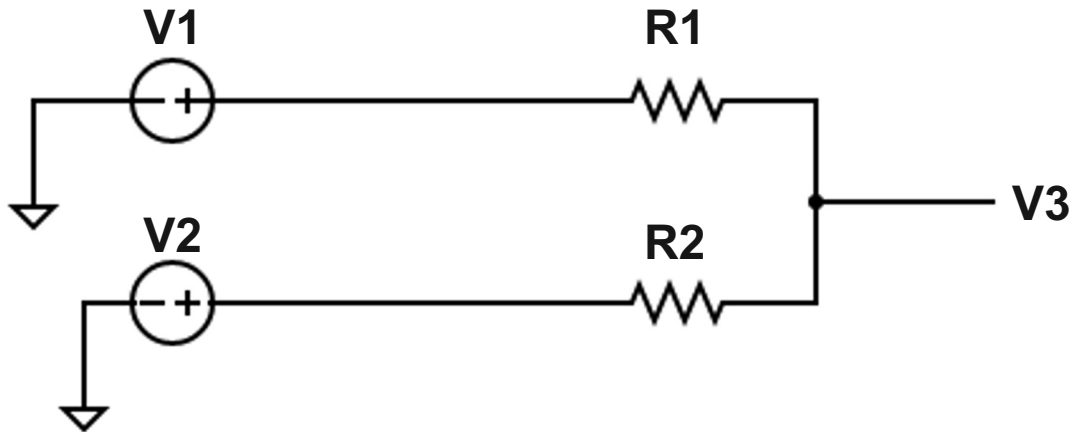The classical demo in telecommunications: noise resistance




© 2021 Circuit Diagram

$$V3 = V1 \frac{R2}{R1+R2} + V2 \frac{R1}{R1+R2}$$

- Two problems in telecommunications:
- Signals degrade over long distance.
 - Noises introduced by... a lot of the things.

Why go digital? – the EE version

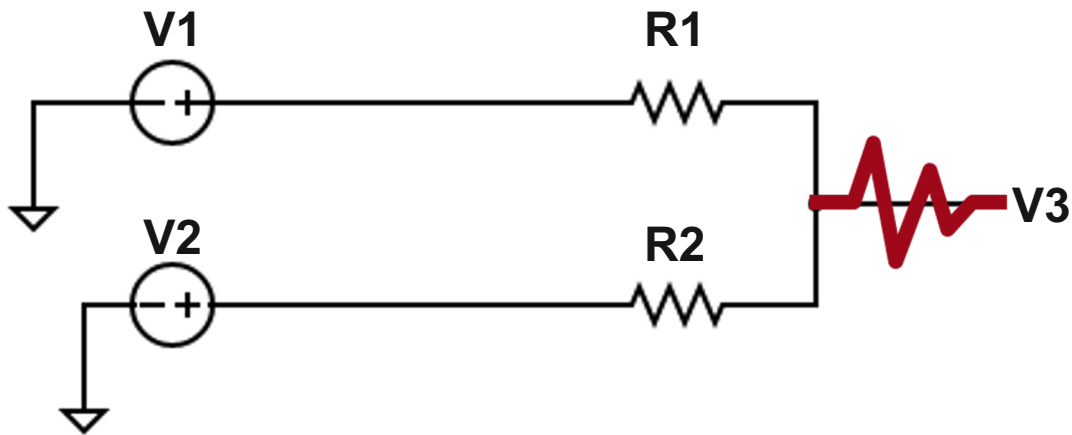The classical demo in telecommunications: noise resistance



© 2021 Circuit Diagram

$$V3 = V1 \frac{R2}{R1+R2} + V2 \frac{R1}{R1+R2}$$



We can AMP signals along the way... but not forever.




Why go digital? – the EE version

The classical demo in telecommunications: the very foundation of the digital abstraction

“Sender”/Input

“Receiver”/Output

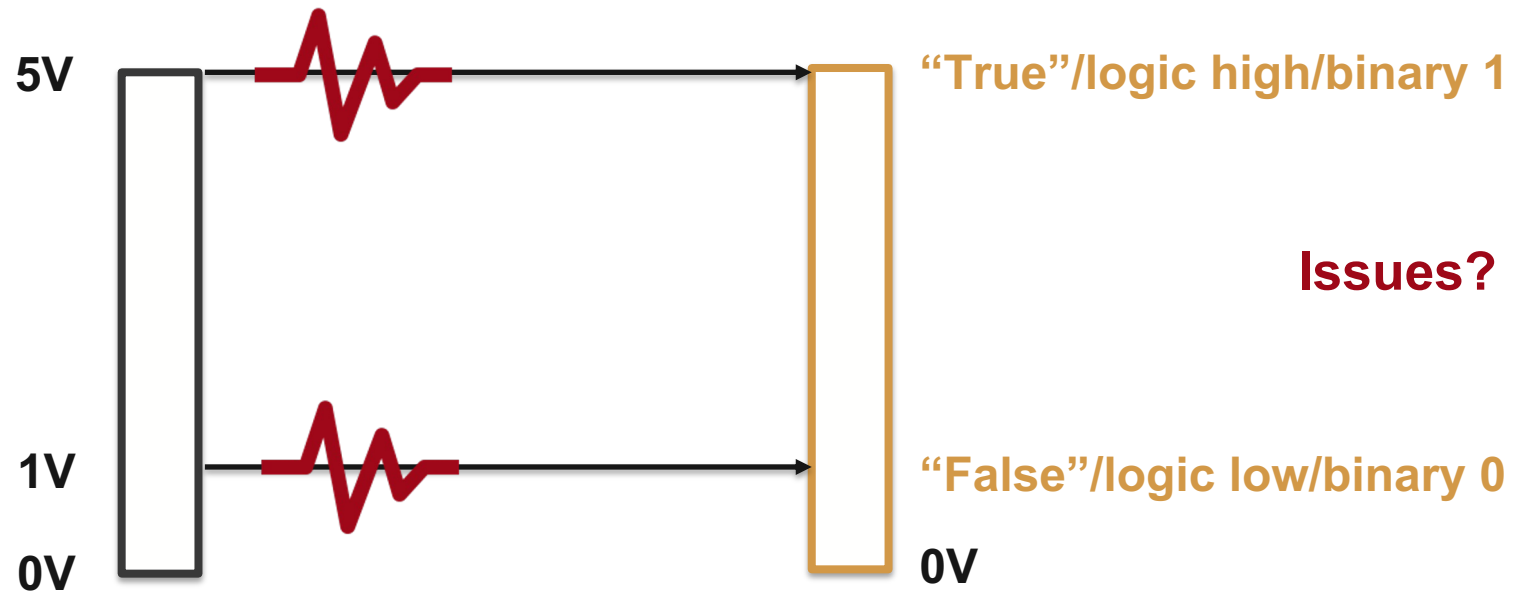


Why go digital? – the EE version

The classical demo in telecommunications: the very foundation of the digital abstraction

“Sender”/Input

“Receiver”/Output

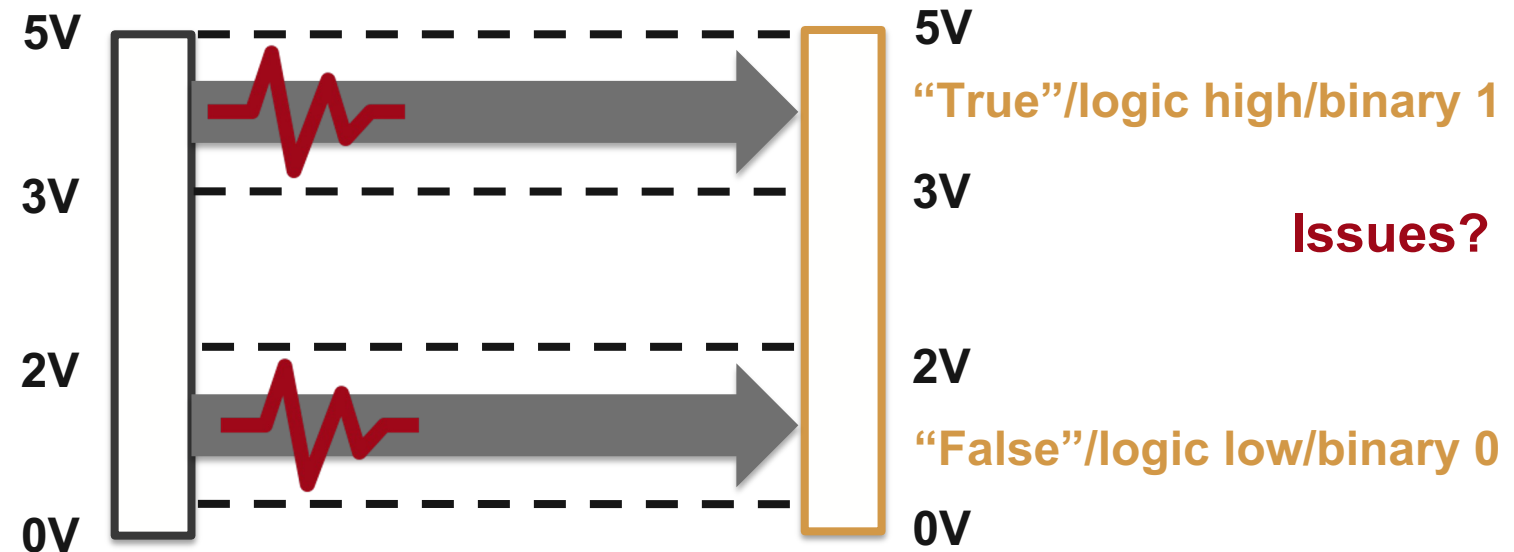


Why go digital? – the EE version

The classical demo in telecommunications: the very foundation of the digital abstraction

“Sender”/Input

“Receiver”/Output

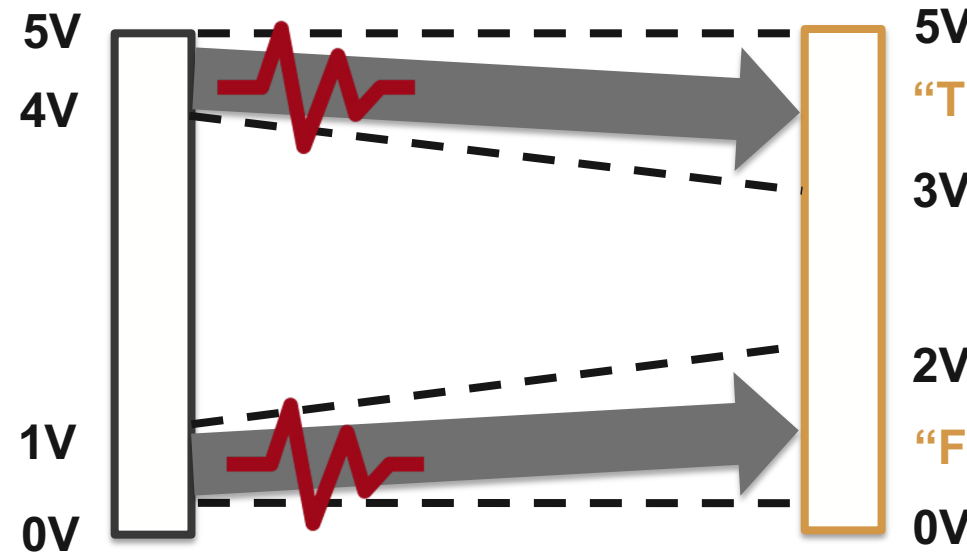

“True”/logic high/binary 1

Now we have some
tolerance to
error/noise margin.

“False”/logic low/binary 0




COE COLLEGE®

Why go digital? – the EE version


The very fundamental of the digital abstraction: the static discipline $V_{OL} < V_{IL} < V_{IH} < V_{OH}$

“Sender”/Input


“Receiver”/Output

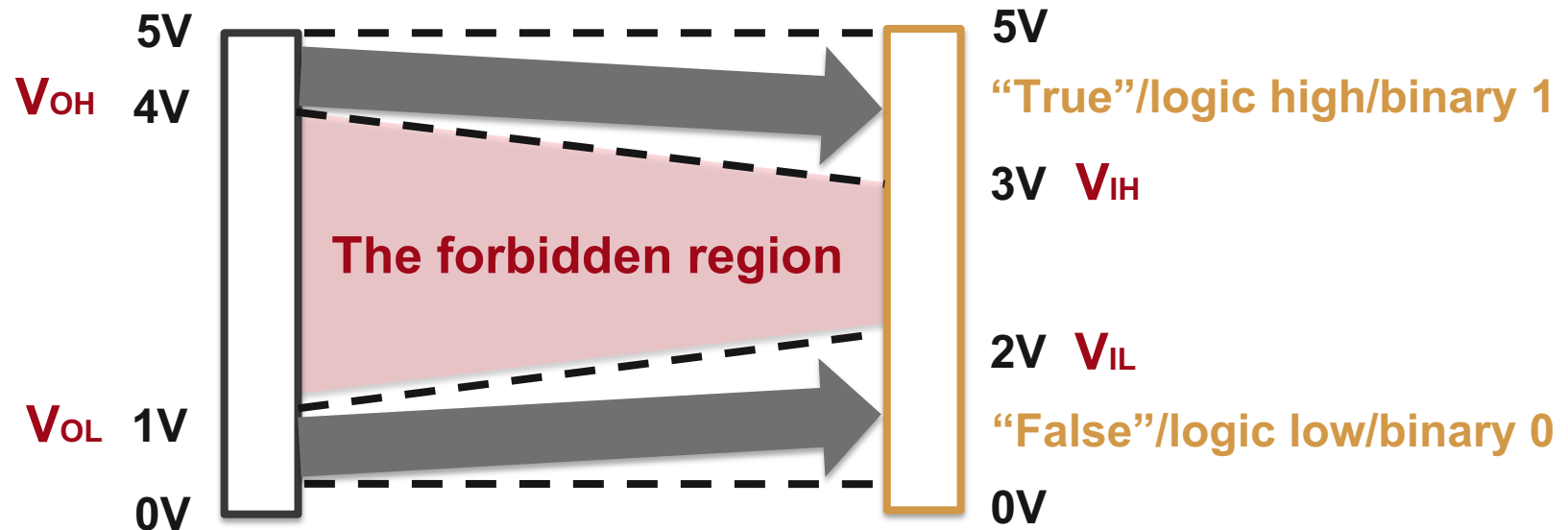

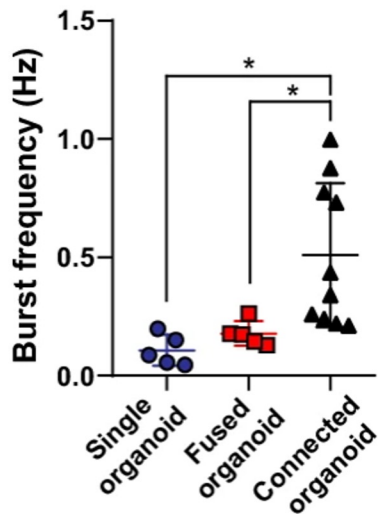
A good spreading
between signals/data is
how engineering works!



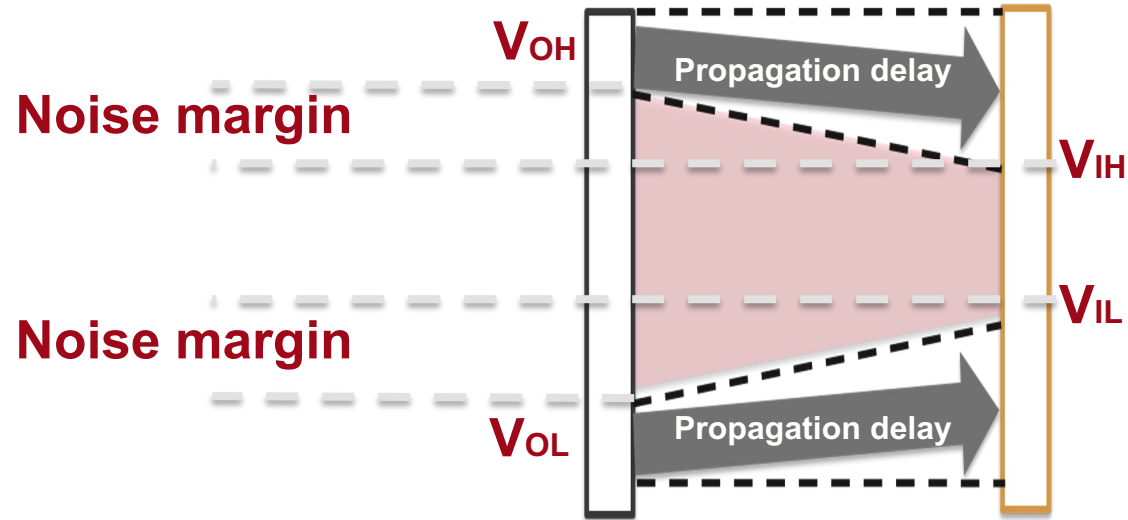
Technicality with this digitizing (quantizing)




Voltage transfer characteristics

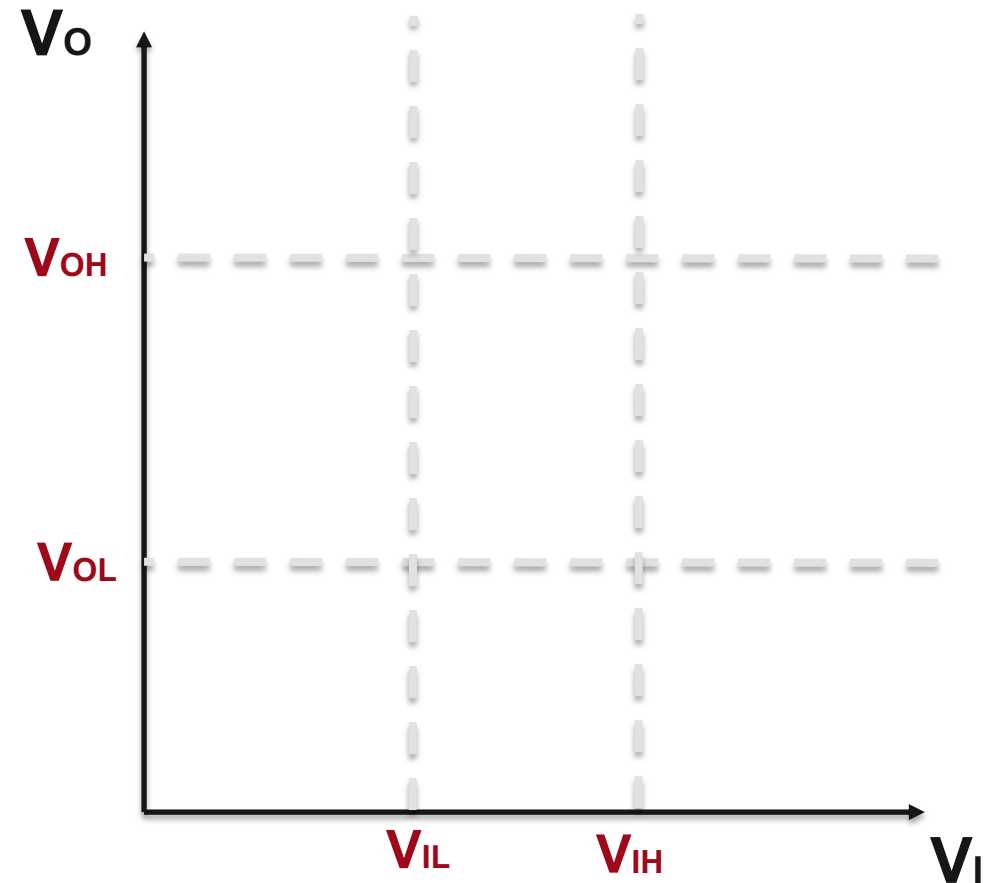

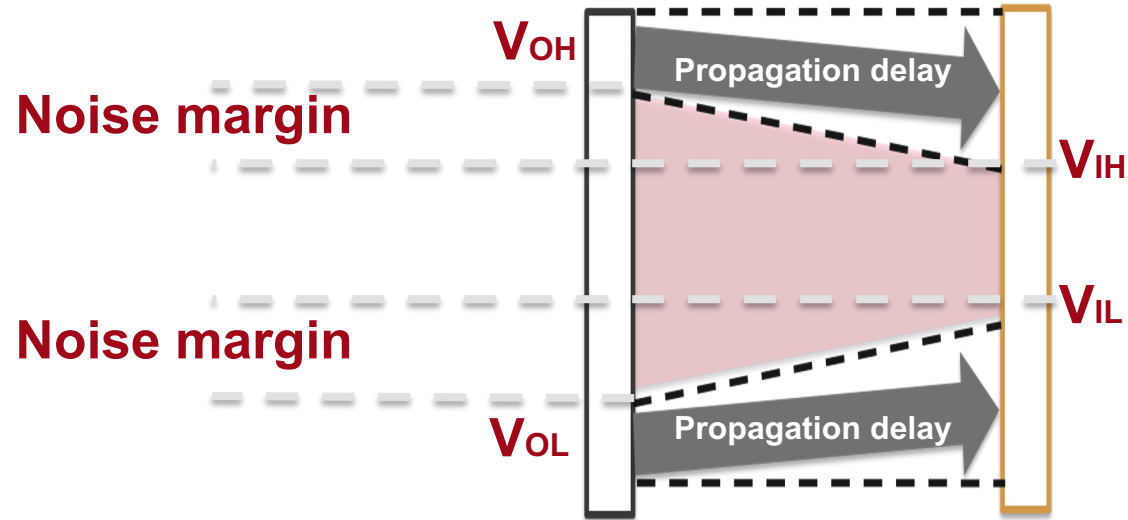
Technicality with this digitizing (quantizing)




Voltage transfer characteristics

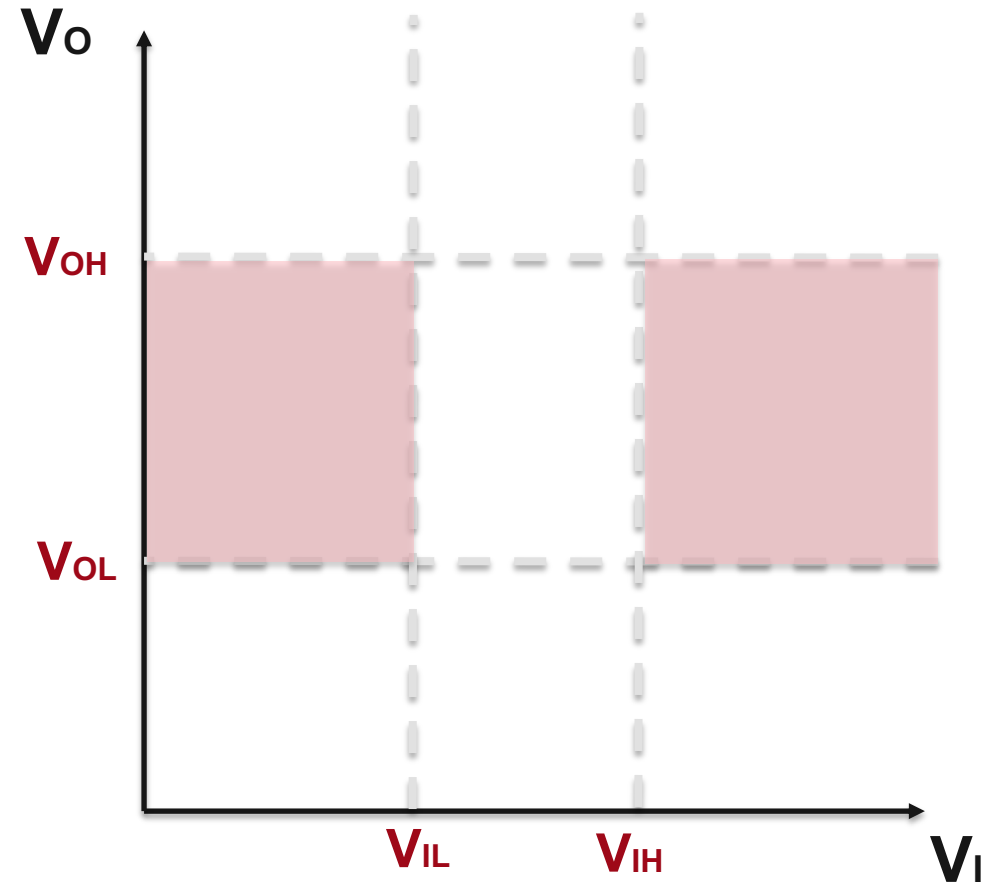

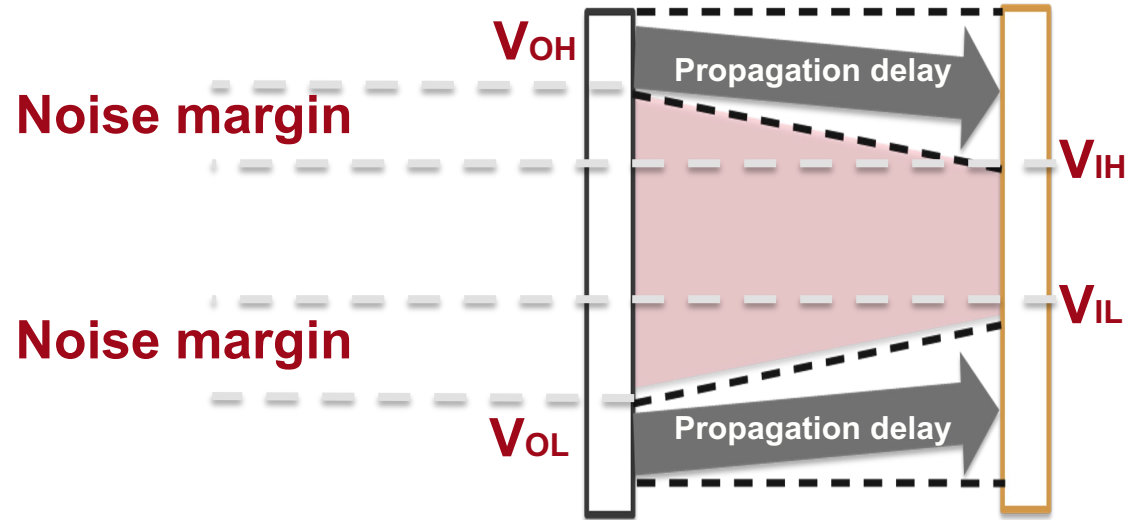
Technicality with this digitizing (quantizing)




Voltage transfer characteristics (VTC)

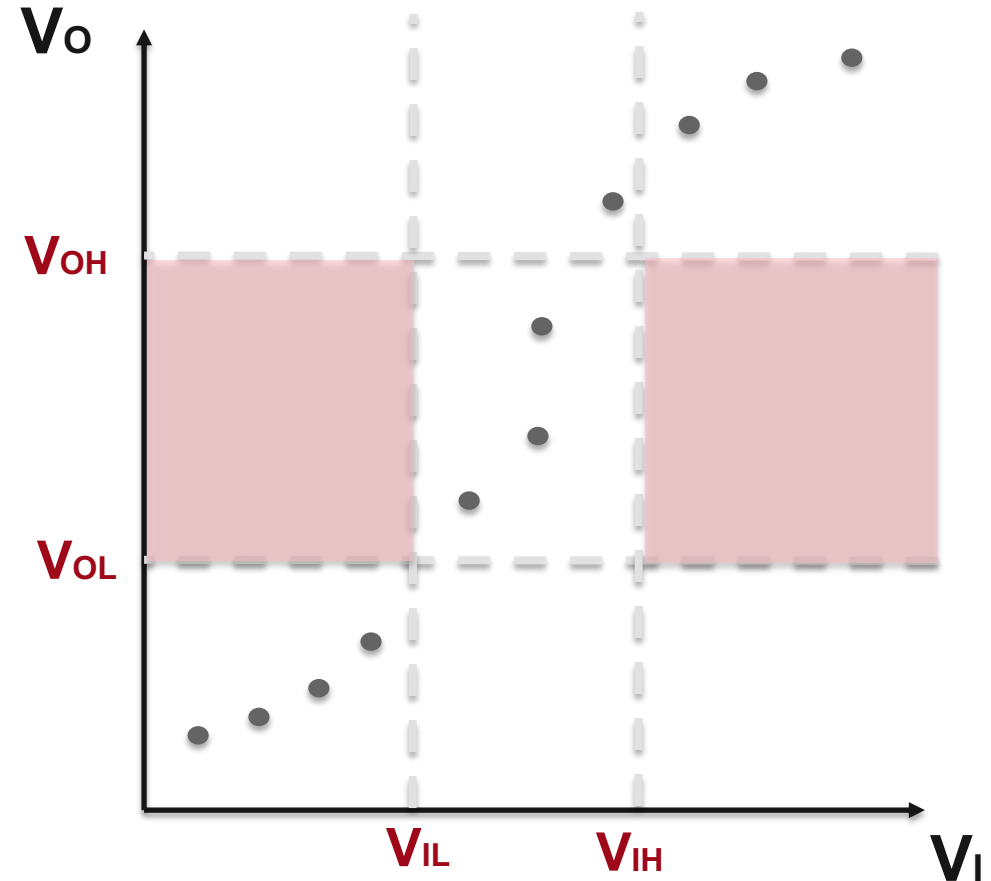

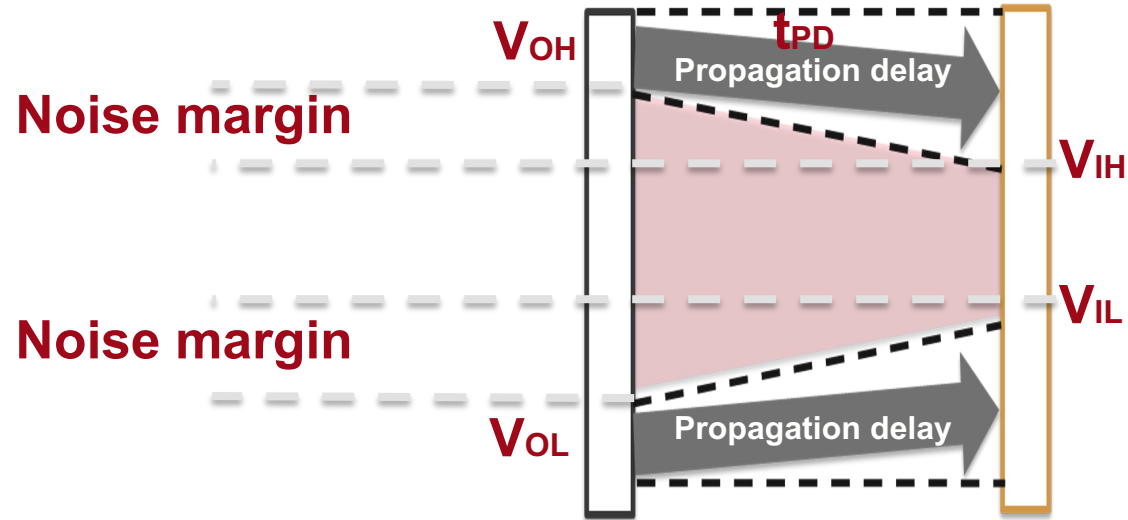Technicality with this digitizing (quantizing)





Voltage transfer characteristics (VTC)

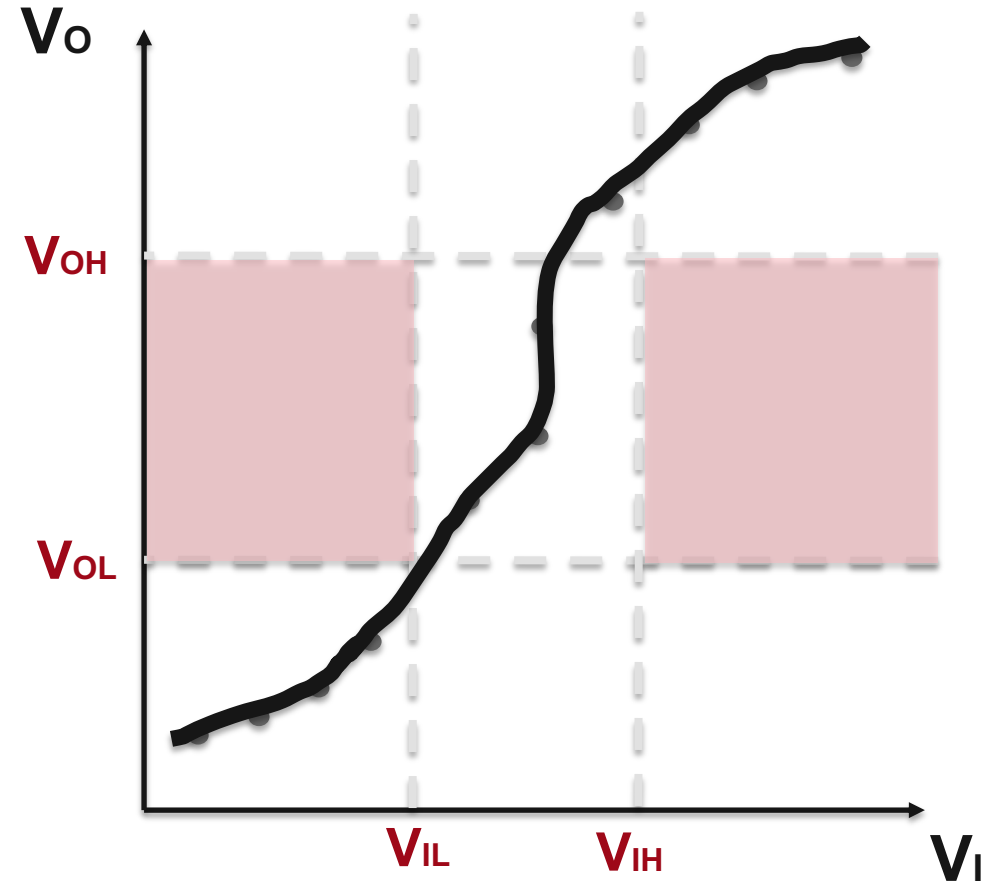

COE COLLEGE®

Not all I/O can satisfy the static discipline, and it won't be linear.

Static discipline example

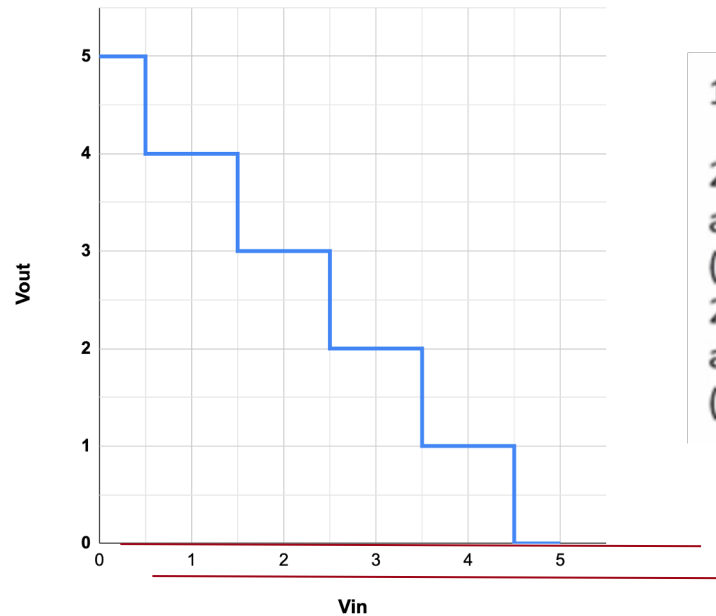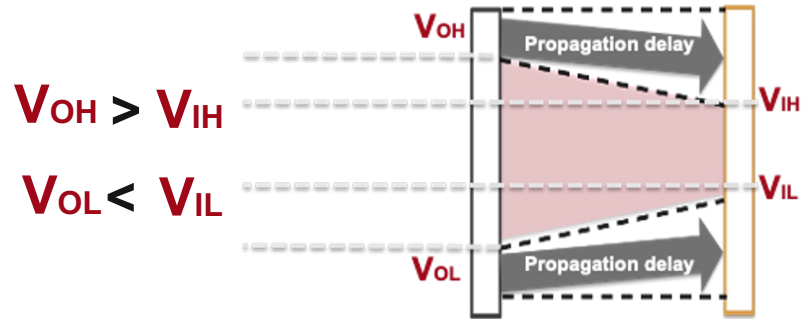

$$1) V_{ol} < V_{il} \leq V_{ih} < V_{oh}$$

2a) Does a valid low input ($V_{in} < V_{il}$) always produce a valid high output ($V_{out} > V_{oh}$)?

2b) Does a valid high input ($V_{in} > V_{ih}$) always produce a valid low output ($V_{out} < V_{ol}$)?

	Vol	Vil	Vih	Voh	Obeys Static Discipline	
Specification #1	0.1	0.4	4.6	4.9	Yes	No
Specification #2	0.6	0.9	4.1	4.4	Yes	No
Specification #3	1.1	1.4	3.6	3.9	Yes	No




If you follow the static discipline, a valid input will always produce a valid output.



COE COLLEGE

Practical digitizing (quantizing)

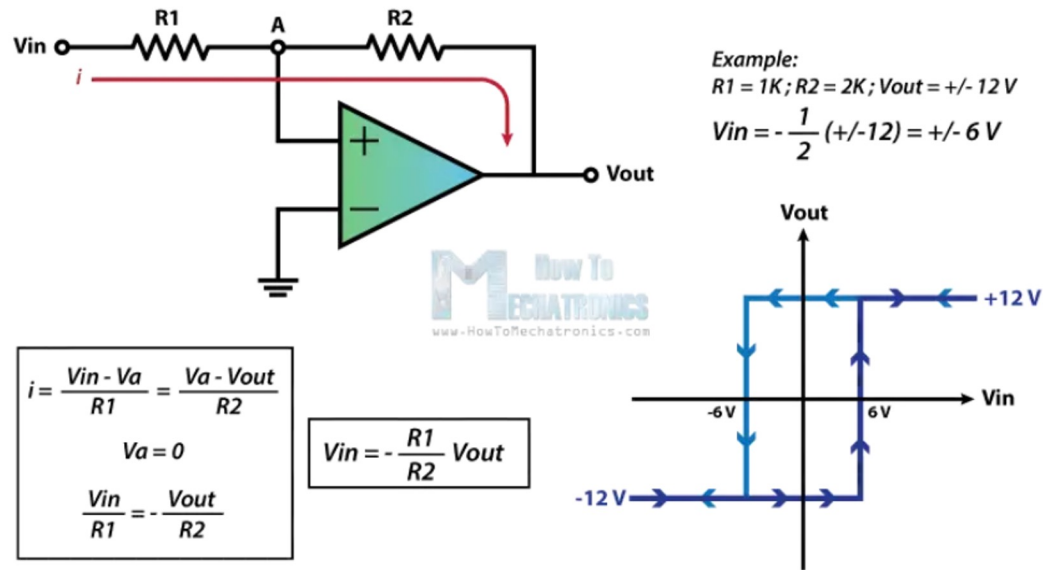

Non-Symmetrical Schmitt Trigger


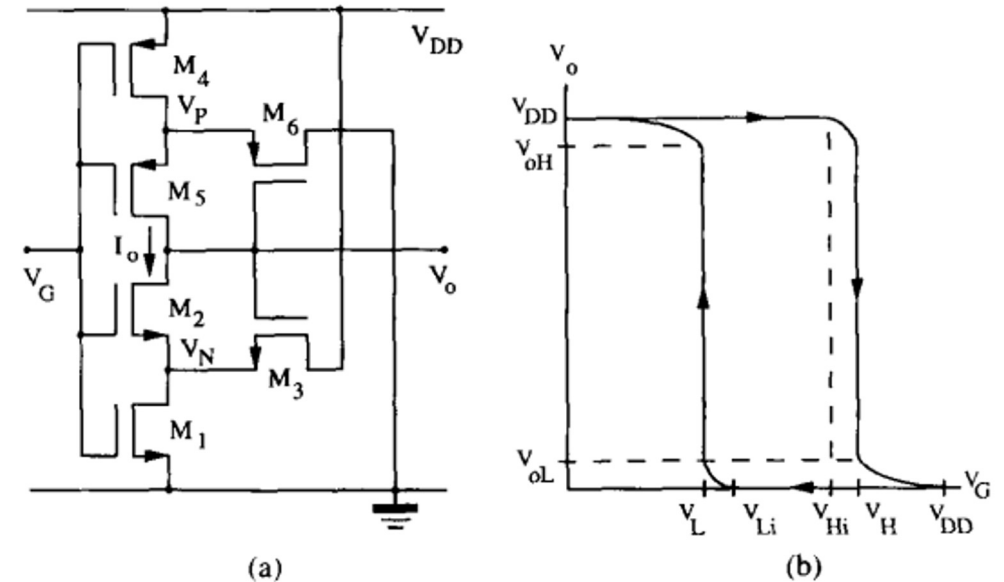


Fig. 1. CMOS Schmitt trigger and its transfer characteristic.

Filanovsky, I. M., and H. Baltes. "CMOS Schmitt trigger design." *IEEE Transactions on Circuits and Systems I: Fundamental Theory and Applications* 41.1 (1994): 46-49.

Why go digital? – the EE version

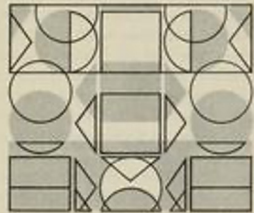So now we can have stable 1s and 0s (in theory), so what?



THE MATHEMATICAL THEORY OF COMMUNICATION

by Claude E. Shannon and Warren Weaver

THE UNIVERSITY OF ILLINOIS PRESS • URBANA • 1963

It doubtless seems queer, when one first meets it, that information is defined as the *logarithm* of the number of choices. But in the unfolding of the theory, it becomes more and more obvious that logarithmic measures are in fact the natural ones.



COE COLLEGE®